

Download File PDF Question Paper Sample For Housekeeping

#Jenny



Finally I get this ebook, thanks for all these I can get now!

#Rio



Cool! I'am really happy

#Markus Jensen



I did not think that this would work, my best friend showed me this website, and it does! I get my most wanted eBook

#Hun Tsu



wtf this great ebook for free?!

#Che Salsa



My friends are so mad that they do not know how I have all the high quality ebook which they do not!

#Diego Butler



so many fake sites. this is the first one which worked! Many thanks

Scheme - E

Sample Question Paper

Course Name : Electrical Engineering Group
Course Code : EE.EP
Semester : Sixth
Subject Title : Power Electronics and Drives
Marks : 100
Time: 3 Hrs.

12232

Instructions:

1. All questions are compulsory
2. Illustrate your answers with neat sketches wherever necessary
3. Figures to the right indicate full marks
4. Assume suitable data if necessary
5. Preferably, write the answers in sequential order

Q.1 A) Attempt any THREE of the following: 12 Marks

- a) Describe the construction of SCR with neat sketch also draw it's symbol.
- b) State & explain the specification of SCR.
- c) List the factors required for selection of heat sink used for SCR.
- d) Draw and explain the characteristics of SCR.

Q.1 B) Attempt any ONE of the following: 06 Marks

- a) Describe the step up and step down chopper with neat diagram.
- b) Explain with waveforms the constant & variable frequency system for chopper control.

Q.2 Attempt any FOUR of the following: 16 Marks

- a) Draw circuit diagram of single phase fully controlled Full wave converter with RL load & explain it's working.
- b) What is the effect of source impedance on performance of 1 phase fully controlled bridge converter?
- c) Draw circuit diagram 3 phase fully controlled bridge converter with R-L load.
- d) Differentiate between single and three phase controlled converter on the basis of no. of SCR, current capacity, application and cost.
- e) Draw neat diagram of cycloconverter for speed control of 3 phase induction motor.
- f) Describe the operation of speed controls of 3 phase induction motor using variable frequency variable voltage method.

[Download PDF version of :](#)
[Question Paper Sample For Housekeeping](#)